



International Centre for Free and Open Source  
Software

## Implementing a NAND Gate with Arduino Uno.

AMAL C THOMAS

# Contents

|          |                                   |          |
|----------|-----------------------------------|----------|
| <b>1</b> | <b>INTRODUCTION</b>               | <b>3</b> |
| <b>2</b> | <b>NAND Gate</b>                  | <b>4</b> |
| <b>3</b> | <b>COMPONENTS USED</b>            | <b>4</b> |
| 3.1      | Hardware Components: . . . . .    | 4        |
| 3.1.1    | Arduino Uno: . . . . .            | 4        |
| 3.1.2    | LEDs: . . . . .                   | 4        |
| 3.1.3    | Push Buttons: . . . . .           | 5        |
| 3.1.4    | Resistors: . . . . .              | 5        |
| 3.2      | Software Components: . . . . .    | 5        |
| 3.2.1    | Arduino IDE: . . . . .            | 5        |
| <b>4</b> | <b>HARDWARE CONNECTIONS SETUP</b> | <b>6</b> |
| <b>5</b> | <b>RESULT</b>                     | <b>7</b> |

# 1 INTRODUCTION

This documentation presents a comprehensive guide for implementing a NAND gate using an Arduino Uno microcontroller. A NAND gate is a fundamental logic gate in digital electronics that performs the logical operation of negation and conjunction. In this setup, we will utilize the Arduino Uno along with LEDs and push buttons to physically demonstrate the functionality of a NAND gate. The project aims to provide a practical understanding of logic gates and microcontroller interfacing, offering a hands-on learning experience for enthusiasts and beginners in electronics and programming. By following this guide, readers will learn how to wire the circuit, program the Arduino, and observe the behavior of the NAND gate in action.

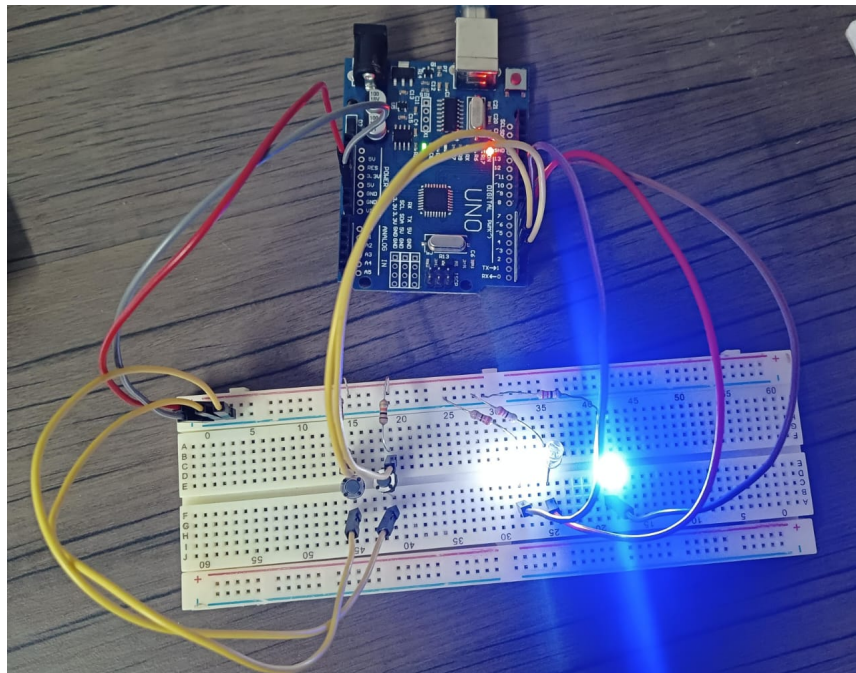


Figure 1

## 2 NAND Gate

A NAND gate is a fundamental digital logic gate that performs the logical operation of negation followed by conjunction. In simpler terms, it produces an output of LOW (0) only when both of its inputs are HIGH (1), and for all other input combinations, it produces an output of HIGH (1). The name "NAND" stands for "Not AND," indicating that the output is the negation of the logical AND operation.

NAND gates are widely used in digital circuits for their versatility and simplicity. They can be used as building blocks for constructing more complex logic circuits, such as flip-flops, latches, and multiplexers. In practical applications, NAND gates are often preferred over other gates due to their functional completeness, meaning that any logical function can be implemented using only NAND gates.

| Input A | Input B | Output |
|---------|---------|--------|
| 0       | 0       | 1      |
| 0       | 1       | 1      |
| 1       | 0       | 1      |
| 1       | 1       | 0      |

Table 1: Truth Table for NAND Gate

The truth table above illustrates the behavior of a NAND gate for all possible input combinations. As shown, the output is 1 (HIGH) for the first three combinations of inputs, and it is 0 (LOW) only when both inputs are 1. This behavior is consistent with the logic described earlier, where the NAND gate produces an output of 0 only when both inputs are 1, otherwise, it produces an output of 1.

## 3 COMPONENTS USED

### 3.1 Hardware Components:

#### 3.1.1 Arduino Uno:

- Includes 14 digital pins and 6 analog pins.
- Operates at a voltage of 5V.
- Microcontroller: ATmega328P
- Uses the ATmega328P microcontroller.
- Runs at a clock speed of 16MHz.

#### 3.1.2 LEDs:

- Light-emitting diodes.
- Typically operate at a voltage of around 2-3 volts.
- Require a current-limiting resistor to prevent damage.

### **3.1.3 Push Buttons:**

- Momentary switches.
- Control the input signals.
- Connected using pull-up resistors for stable operation

### **3.1.4 Resistors:**

- 330 Ohm resistors.
- Used for current limiting with LEDs.
- 10k Ohm pull-up resistors.
- Ensure stable signal reading with push buttons.

## **3.2 Software Components:**

### **3.2.1 Arduino IDE:**

- Integrated Development Environment (IDE) for Arduino boards.
- Provides a user-friendly interface for writing, compiling, and uploading code to the Arduino Uno.
- Offers a wide range of built-in functions and libraries for interfacing with hardware components.

## 4 HARDWARE CONNECTIONS SETUP

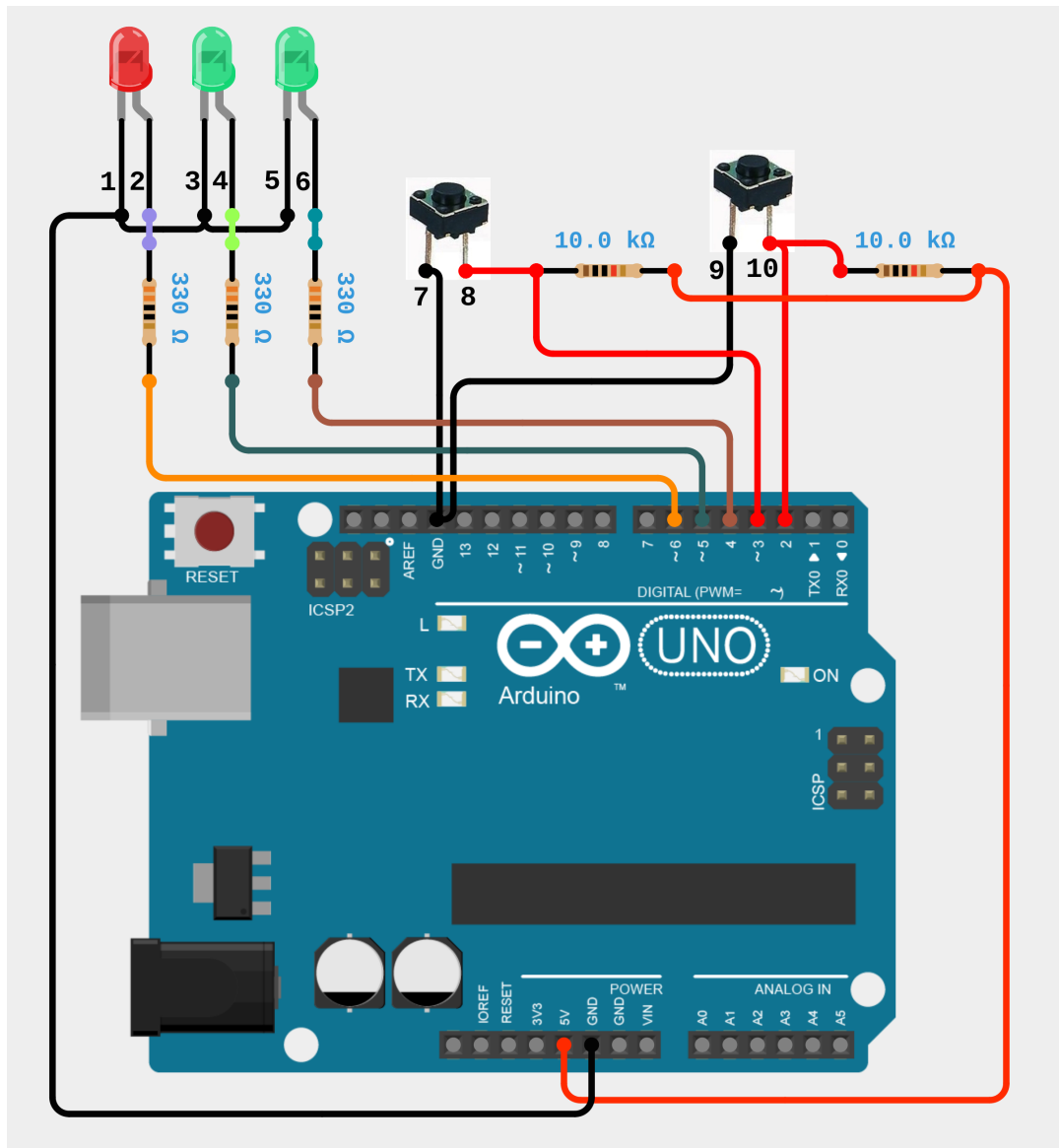


Figure 2: Hardware Connections Setup Circuit Diagram

1. Connect the negative (-) terminal of the result LED to the ground (GND) of the Arduino Uno.
2. Connect the positive (+) terminal of the result LED to digital pin 6 of the Arduino Uno through a 330 Ohm resistor.
3. Connect the negative (-) terminal of input 1 LED to the ground (GND) of the Arduino Uno.
4. Connect the positive (+) terminal of input 1 LED to digital pin 5 of the Arduino Uno through a 330 Ohm resistor.
5. Connect the negative (-) terminal of input 2 LED to the ground (GND) of the Arduino Uno.
6. Connect the positive (+) terminal of input 2 LED to digital pin 4 of the Arduino Uno through a 330 Ohm resistor.

7. Connect one terminal of push button 1 to the ground (GND) of the Arduino Uno.
8. Connect the other terminal of push button 1 to digital pin 3 of the Arduino Uno. Also, connect this end to +5V of the Arduino Uno through a 10K ohm resistor.
9. Connect one terminal of push button 2 to the ground (GND) of the Arduino Uno.
10. Connect the other terminal of push button 2 to digital pin 2 of the Arduino Uno. Also, connect this end to +5V of the Arduino Uno through a 10K ohm resistor.

## 5 RESULT

The implemented NAND gate circuit using Arduino Uno and LEDs demonstrated the expected behavior of toggling the state of the LEDs when the push buttons were pressed. The input LEDs accurately reflected the state of the corresponding push buttons, toggling between HIGH and LOW states with each press. When both input push buttons were pressed simultaneously, the output LED remained in the LOW state, consistent with the truth table of a NAND gate. The circuit operated reliably, and no unexpected behavior was observed during testing.